
# Verilog Lab 1 – 4-Bit ALU with 2 Instructions

#### I. 4-Bit ALU with 2 Instructions:

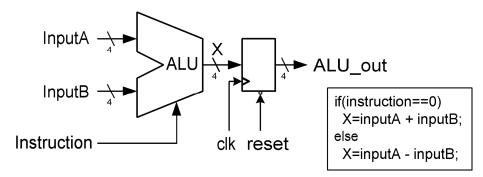

### II. Objectives:

In this lab, you will learn:

- 1. A synthesizable Verilog HDL code and the corresponding test bench.
- 2. How to run NC-Verilog simulator?

#### III. Lab Files:

- 1. Upload your files (Lab1.tar) into your work directory by FTP.
- 2. Type this command to extract your files.

#### tar -xvf Lab1.tar

3. Lab1 files are shown as below:

Filename	Description
Lab1_alu.v	RTL code for this ALU
Lab1_test_alu.v	Test bench for this ALU
Lab1_alu_run.f	Command-line file
Lab1_test_alu_file.v	Test bench with file I/O
program.txt	Input stimulus
program_out.txt	Correct answers

4. Your ALU module looks like this

```
module ALU(alu_out,instruction,inputA,inputB,clk,reset); output [3:0] alu_out; input [3:0] inputA,inputB; input instruction; input clk,reset;
```

...

5. Type this command to enter Lab1 directory:

cd Lab1

### IV. Environment Setup:

1. Source the default *cshrc* file:

source /usr/cadence/cshrc

### V. Module Description:

This RTL describes a simple ALU with two 4-bit input signals and 2 instructions. One instruction is summation, and the other one is subtraction.

#### VI. Check Verilog Code by NC-Verilog:

1. Type this command

ncverilog Lab1\_alu.v

- 2. NC-Verilog will report one error because the signal X is not declared. Please help to add the declaration for the file Lab1\_alu.v.
  - Type this command to enter text editor

```
gedit Lab1_alu.v
```

Declare signal X:

```
reg [3:0] alu_out;
reg [3:0] X; // add this line
```

3. Run the command in step 1 again. No error should occur now.

### VII. Run simulation with a test bench by NC-Verilog:

1. Type this command

```
ncverilog Lab1_test_alu.v Lab1_alu.v
```

- 224 errors are found after simulation. Please read the file alu\_out.txt to find out what happens. Please modify the file Lab1\_alu.v to fix these errors.
  - Type this command to enter text editor

```
gedit Lab_alu.v
```

Correct the computing

```
If (!instruction)
X=inputA+inputB;
else
X=inputA-inputB;
```

- 3. Run the command in step 1 again. The simulation result is correct now.
- 4. Instead of the command in step 1, you can also use the command-line file to run simulation by typing this command

```
ncverilog -f Lab_alu_run.f
```

### VIII. Run simulation with file I/O:

Using the test bench Lab1\_test\_alu\_file.v for simulation. Can you find out how this test bench works with file I/O?

```
$ readmemb("program.txt", program);  // Input stimulus
$ readmemb("program_out.txt", answer);  // Correct answers
```

#### IX. Checkpoints:

Please check with TAs before leaving this lab to make sure the following goals are accomplished and to get credits.

- 1. Please fix the declaration error in Section VI.
- 2. Please fix the simulation errors in Section VII.

```
ncsim> source /usr/cad/cadence/IUS/cur/tools/inca/files/ncsimrc
ncsim> run
Congratulations!! Your Verilog Code is correct!!
Simulation complete via $finish(1) at time 10260 NS + 0
```

# **END of LAB**

# Creator:

1st Edition: Chao-Tsung Huang, 2002 2nd Edition: Yu-Lin Chang, 2004 3rd Edition: Yu-Lin Chang, 2005 4th Edition: En-Jui Chang, 2010 5th Edition: En-Jui Chang, 2011 6th Edition: Yu-Min Lin,2013 7th Edition: Chou Ching Yao,2015